
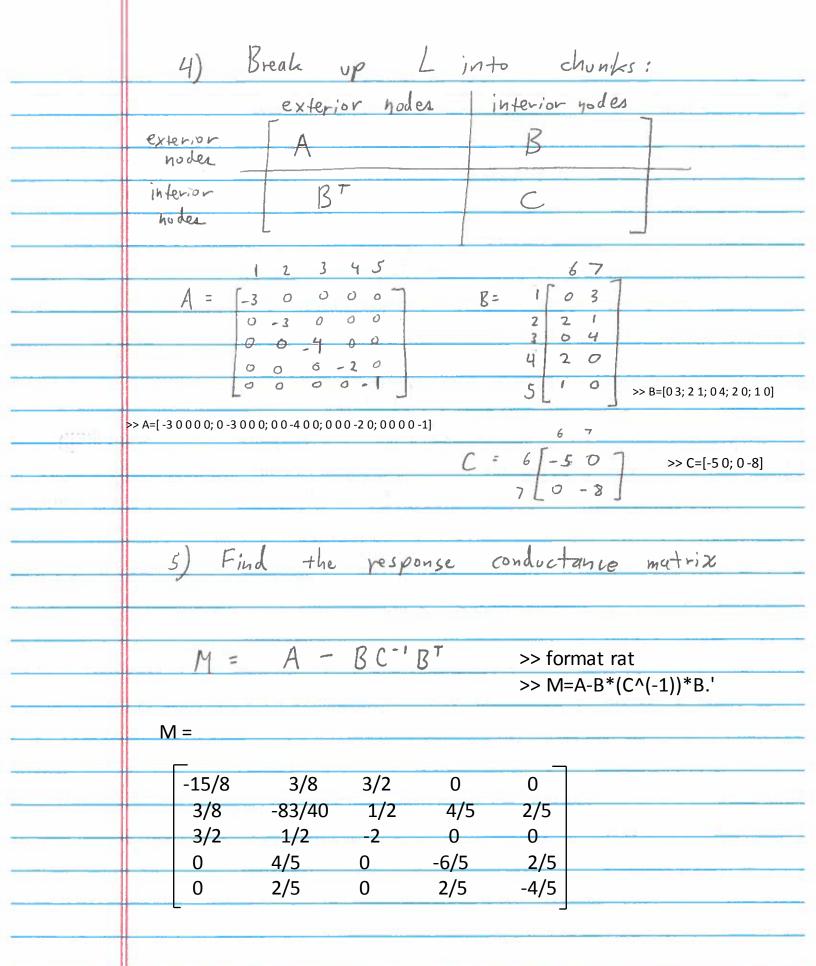
The experiments. 1) Make up a non-planar network (5) 6 Assign positive numbers to each wire; conductances 3) Make a matrix called 2 600 K off -diagonal diagonal 3 entry Lij 0 entry Lii ~ 2 = conductance 0 20 = negative 0 of wire (i) to (j) 0 sum of wires 2 -50 (o if no direct 0 2 0 fouching (i) 1 connection) 4



	6) Check that some circular minors
	of M gre negative.
	J
	Circular minor:
3-2-3-2	(a) choose any two sets of
	the exterior nodes, both
	in order on the circle,
	non-interlaced (I can circle
/	them separately!) both with
	1 same number k of nodes
	9 (
	(5) ex: (k=3)
	(8)
	O
	(b) Pich either set, and use its
	numbers to choose k rows of M
	(Easiert: pick the one that
	doesn't wrap around the circle buck to 1)
	R= rows: {2,4,5}=R, in increasing order.
	(c) Across from each node in R,
	1 (2) in the circle, is a node in the
	(a) (4) other set G, standing for a column
	(9) (3) of M. Choose those columns,
	in the order from their
	matching with R; G= {1,9,8}
	to make a smaller matrix M(R,G)
	(d) E. J (a) K I I M (D C)
	(d) Find (-1) h det M(R,G).

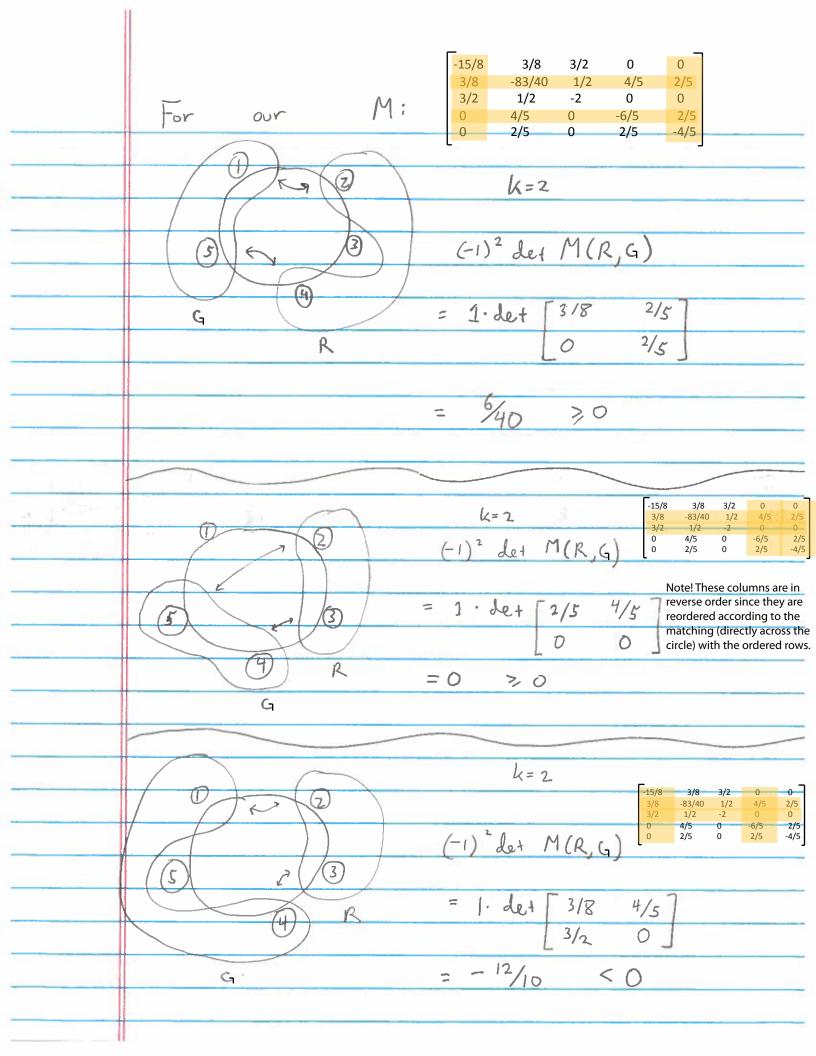

7)	Next: For each four nodes, let
	the other remaining nodes be pushed
	inside the circle.
	Then repeat steps 1) through 6),
2.1 12 10 122 0	with the exterior noder just the four and
	interior now including the others.
	To make L, A, B, C, ; list the pushed
7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7	nodes very last.
	ex: push node 3
	(Leep D D D D D)
	1 2 3
	New L=
	① ② ④ ⑤ Ø Ø ③
	D - 3 0 0 0 0 3 6
A	(2) 0 -3 0 0 2 1 0 B
	G 0 0 -2 0 2 0 0
-	
n T	
B^{T}	
	36000004-4
	Find new M = A - B C BT
	I ma new mi - A BCB
	Test circular minors: We expect that there
	will be four noder from original that give negatives!